

TEST

- Conceptual
  - electric force
  - connecting ammeters and voltmeters
  - circuits
- Problems
  - Coulomb's Law
  - Series-only circuit(s)
  - Parallel-only circuit(s)

Review

## • Electric force

- Like charges repel ; unlike charges attract

- Coulomb's Law:

$$\text{magnitude } F = \frac{k q_1 q_2}{r^2}$$

direction comes from drawing

$$k = 9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}$$

- Circuits

- Ohm's Law  $\rightarrow V = IR$

- Electric Power

$$P = IV = I^2R = \frac{V^2}{R}$$

- Equivalent Resistance


- Series  $\rightarrow R_{eq} = R_1 + R_2 + \dots$

- Parallel  $\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

- Variables: [Units]
  - $F \rightarrow$  force [newtons  $\rightarrow N$ ]
  - $q \rightarrow$  charge [coulombs  $\rightarrow C$ ]
  - $r \rightarrow$  distance between the charges [meters  $\rightarrow m$ ]
  - $V \rightarrow$  electric potential, voltage, voltage drop, potential difference [volts  $\rightarrow V$ ]
  - $I \rightarrow$  current [amperes  $\rightarrow A$ ]
  - $R \rightarrow$  resistance [ohms  $\rightarrow \Omega$ ]
  - $P \rightarrow$  power [watts  $\rightarrow W$ ]
  - $R_{eq} \Rightarrow$  equivalent resistance [ohms  $\rightarrow \Omega$ ]

Problems

1)

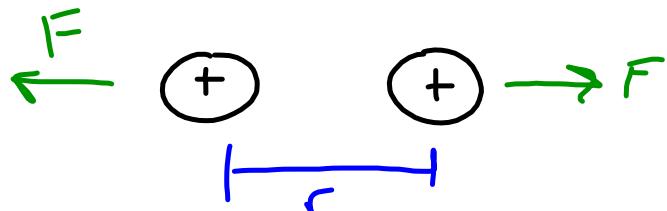

$$F = \frac{kq_1 q_2}{r^2}$$

$$r^2 = \frac{kq_1 q_2}{F}$$

$$r = \sqrt{\frac{kq_1 q_2}{F}}$$

$$= \sqrt{\frac{(9E9 \frac{N \cdot m^2}{C^2})(4E-6 C)(4E-6 C)}{105 N}}$$

$$= 0.037 m$$

$$q_1 = 4E-6 C$$


$$q_2 = 4E-6 C$$

$$F = 105 N$$

$$k = 9E9 \frac{N \cdot m^2}{C^2}$$

$$r = ?$$

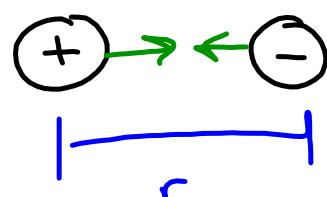Two charges, separated by a distance of 0.05 m, exert a force of 20 N on each other. One charge has a value of  $-6 \times 10^{-6}$  C; what is the charge of the other one if this charge is positive?



$$\left(\frac{r^2}{kq_1}\right)F = \frac{kq_1q_2}{r^2} \left(\frac{r^2}{kq_1}\right)$$

$$q_2 = \frac{Fr^2}{kq_1}$$

$$F = 20 \text{ N}$$

$$q_1 = -6 \times 10^{-6} \text{ C}$$

$$q_2 = ?$$

$$k = 9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}$$

$$r = 0.05 \text{ m}$$


- Make the force negative  
to make  $q_2$  positive

$$= \frac{(-20 \text{ N})(0.05 \text{ m})^2}{(9 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2})(-6 \times 10^{-6} \text{ C})}$$

$$= 9.26 \times 10^{-7} \text{ C}$$

## Circuits

7) a.

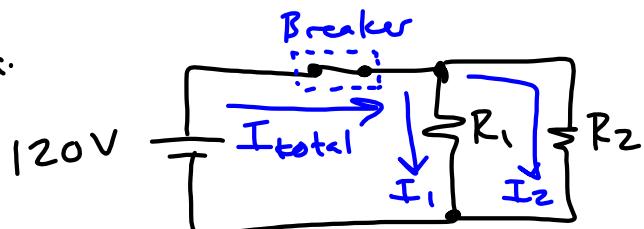 $R_1 \rightarrow$  blander $R_2 \rightarrow$  coffee makerBreaker opens when  
 $I_{\text{total}} > 15\text{A}$ 

$$V_1 = V_2 = 120\text{V}$$

$$P_1 = 400\text{W}$$

$$P_2 = 900\text{W}$$

$$P_1 = I_1 V_1$$

$$I_1 = \frac{P_1}{V_1}$$

$$= \frac{400\text{W}}{120\text{V}}$$

$$= 3.33\text{A}$$

$$P_2 = I_2 V_2$$

$$I_2 = \frac{P_2}{V_2}$$

$$= \frac{900\text{W}}{120\text{V}}$$

$$= 7.5\text{A}$$

$$I_{\text{total}} = I_1 + I_2 = 10.83\text{A}$$

$$\text{Add a device} \rightarrow 15\text{A} - 10.83\text{A} = 4.17\text{A}$$

$$P_{\text{extra device}} = I_{\text{extra device}} V$$

$$= (4.17\text{A})(120\text{V})$$

$$= 500\text{W}$$