

## LAB - RC CIRCUITS

- Determine the relationship between current and time for three different resistor values with one capacitor.
- Whiteboard:
  - Resistor and capacitor values
  - $I$  vs.  $t$  graph  $\rightarrow$  function of best fit

